

香港中文大學 The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lab09: Shift Register in Verilog






Recall: PIPO in VHDL

Recall: Lab03 – PIPO Shift Register



 - A parallel-in-parallel-out (PIPO) shift register is composed of multiplexers (mux) and D-Flip-Flops (D-FF) as follows:
 - It allows parallel input (through either external inputs (Din) or the shifted outputs from previous D-FFs (Q) based on the select signal (sel) at rising edges of clock (clk));
 - It produces parallel output (through external outputs (Q)).



Recall: Lab03 – PIPO Shift Register



- When reset equals to 1:
 - All the Q(s) are reset to zero(s) asynchronously (immediately).
- Otherwise (when reset equals to 0), at every rising edge of clk:
 - When sel is 1, the values of Din are assigned to Q of D-FFs in parallel;
 - Otherwise (when sel is 0), the value kept by each D-FF is shifted to the D-FF on its right.
 - A '0' is shifted into to the "leftmost" D-FF;
 - The value kept by the "rightmost" D-FF is shifted out (i.e., discarded) from the PIPO shift register.

Recall: Lab03 – PIPO Shift Register



Instructions:


- Select the digit using SW 0-3
- Press BTNU and toggle the SW7 at the same time
 - The digit will display on the LED 0-3
- Then toggle the SW7 only
 - The digit will shift left
- Press BTNC to reset the LED 0-3



Shift Left





 

Display digit on the right

Notes on Constraints (XDC file)



 Add the following statement into XDC file when encountering error [Place 30-574].


- The reason is that We bind the signal clk to a switch, which is not a real clock.
- This statement is also required for Verilog project.


```
architecture arch_dff of D_FF is begin process (clk, reset) begin if reset = '1' then Q <= '0'; elsif rising_edge(clk) then Q <= D; end if; end process; end arch_dff;
```

Little Problem: Glitch



  If you switch once SW7 but the SIPO shifts twice, you encounter a glitch.



 

- The glitch is caused by the poor switch contact.
 - Operating once (by human) causes multiple positive edge in the signal.
 - It is also called by switch bouncing.



Task: PIPO in Verilog

Lab09: Step-by-Step Instructions (1/2)

- 1. <u>Use the structural design</u> to implement the PIPO shift register in Verilog.
 - You can try to translate your VHDL codes of Lab03 into Verilog.
 - When creating the project, please remember to select Verilog as the target language.



- 2. Create a XDC file with the following assignments:
 - Input: clk = SW7, reset = BTNC, sel = BTNU, D0~D3 = SW0~SW3
 - Output: $Q0 \sim Q7 = LD0 \sim LD7$
 - Add the following statement to your XDC file:

Lab09: Step-by-Step Instructions (2/2)

- 3. Generate the bitstream and download it to Zedboard.
- 4. Toggle SW7 regularly to simulate the **clk** and verify the behavior of your design as follows:
 - ① Set D to "0101", press BTNU and toggle SW7;
 - ② Toggle SW7 only until "0101" move to SW4-7;
 - 3 Set D to "1010", press BTNU and toggle SW7;
 - Then toggle SW7 three more times to shift the digit;
 - S Asynchronously reset PIPO by pressing BTNC.
 - © Record the above verification as a video for submission.
- 5. Submit your source code.
 - Submit the zip file of source codes and verification video to Blackboard.
 - Deadline: 12:30 on 2 Apr. 2025
 - Late submission is NOT acceptable (unless otherwise approved)



香港中文大學

The Chinese University of Hong Kong

Thank You!

