



香港中文大學

The Chinese University of Hong Kong


CENG3430 Rapid Prototyping of Digital Systems
Lab03: Shift Register



Combinational vs. Sequential Circuit



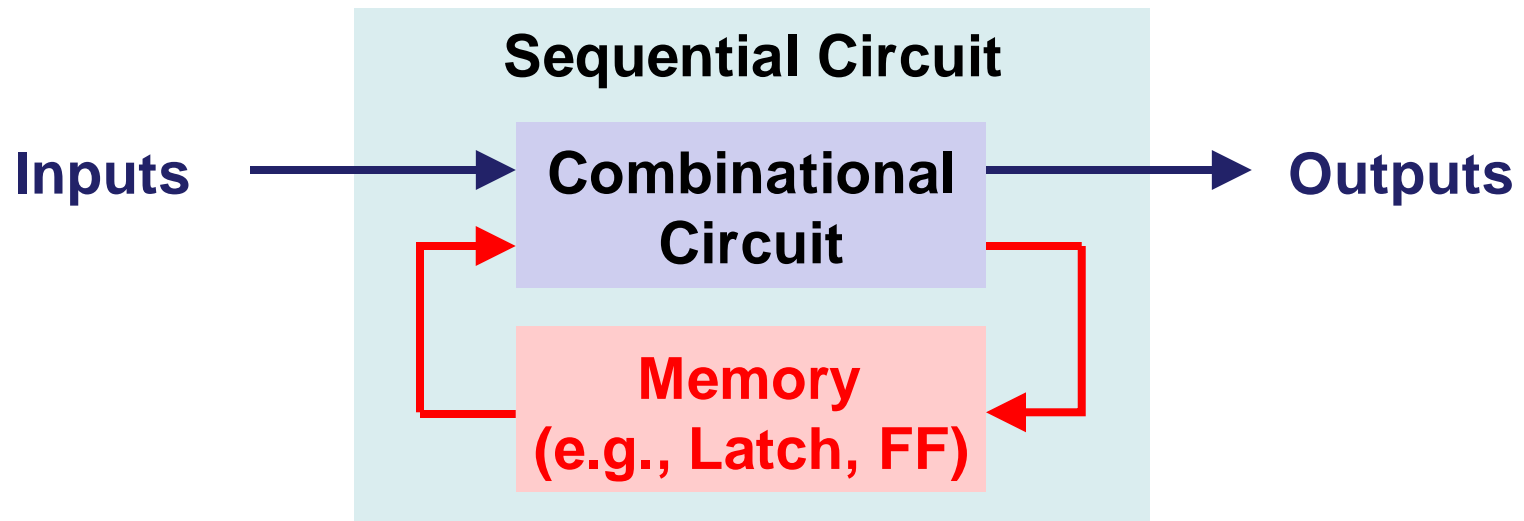
- **Combinational Circuit: no memory**
 - Outputs depend on the *present* inputs only.
 - **Rule:** Use either concurrent or sequential statements.
- **Sequential Circuit: has memory**
 - Outputs depend on *present* inputs and *previous* outputs.
 - **Rule: MUST** use sequential statements (i.e., `process`).



Seq. Circuit Example: Shift Register



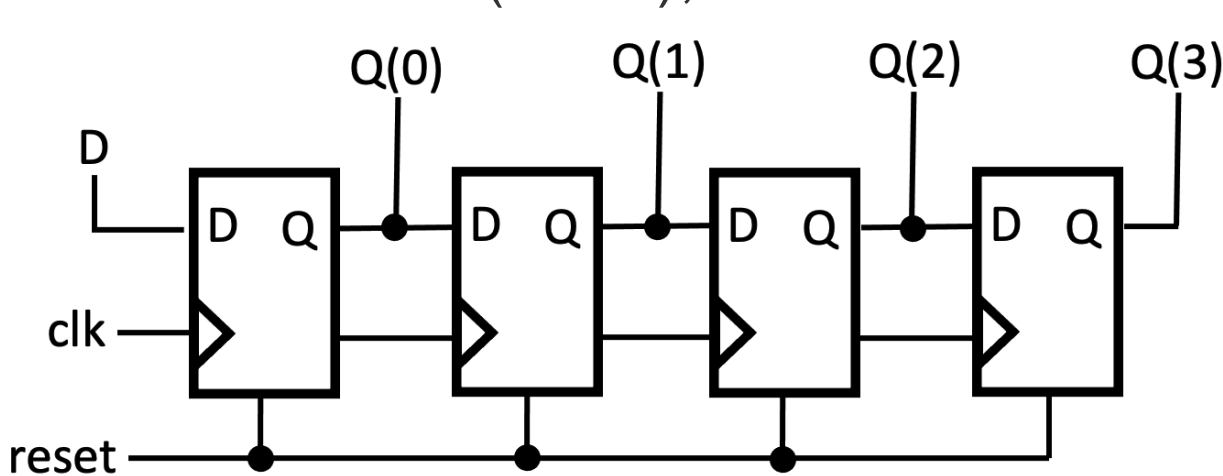- A **register** is a device that can be composed of a group of FFs to store multiple bits of data.
- A **shift register** allows the stored data being moved from one FF to another.
 - There are basically **four** types: ① Serial-In-Serial-Out (SISO), ② Serial-In-Parallel-Out (SIPO), ③ Parallel-In-Serial-Out (PISO), and ④ Parallel-In-Parallel-Out (PIPO).



Ex: Serial-In-Parallel-Out (SIPO) Shift Register



Example: SIPO

SIPO Shift Register in VHDL



entity **sipo** is

```
port (D, clk, reset : in std_logic;  
      Q : buffer std_logic_vector(3 downto 0));  
end sipo;
```

architecture arch_sipo of sipo is


```
component D_FF is  
  port (D, clk, reset : in std_logic;  
        Q : buffer std_logic);  
end component;
```

begin

```
DFF0 : D_FF port map(D, clk, reset, Q(0));  
DFF1 : D_FF port map(Q(0), clk, reset, Q(1));  
DFF2 : D_FF port map(Q(1), clk, reset, Q(2));  
DFF3 : D_FF port map(Q(2), clk, reset, Q(3));
```

end arch_sipo;

 
```
architecture arch_dff of D_FF is  
begin  
  process (clk, reset)  
  begin  
    if reset = '1' then  
      Q <= '0';  
    elsif rising_edge(clk) then  
      Q <= D;  
    end if;  
  end process;  
end arch_dff;
```



Constraints (XDC file)



 - Bind the I/O ports and physical pins as following:
 - Input: clk=SW7, reset=BTNC, D=SW0
 - Output: Q0~Q3 = LD0~LD3



Notes on Constraints (XDC file)



- Signals in the XDC file is case-sensitive.
 - The case of signals should be same with the entity declaration.
 - Because XDC can be also used with Verilog, which is case-sensitive.
- Vector signals in the XDC file are indexed with [] instead of ().

```
set_property PACKAGE_PIN T22 [get_ports Q[0]]; #LD0
set_property PACKAGE_PIN T21 [get_ports Q[1]]; #LD1
set_property PACKAGE_PIN U22 [get_ports Q[2]]; #LD2
set_property PACKAGE_PIN U21 [get_ports Q[3]]; #LD3
```

Q(0) here will be wrong.

```
set_property PACKAGE_PIN F22 [get_ports D]; #SW0
set_property PACKAGE_PIN M15 [get_ports clk]; #SW7
set_property PACKAGE_PIN P16 [get_ports reset];#BTNC
```

Using 'RESET' here will cause an error.

```
# Electrical specification...
```


Notes on Constraints (XDC file)



- Add the following statement into XDC file when encountering error [Place 30-574].

Implementation (3 errors)

Place Design (3 errors)

❗ [Place 30-574] Poor placement for routing between an IO pin and BUFG. If this sub optimal condition is acceptable for this design, you may use the CLOCK_DEDICATED_ROUTE constraint in the .xdc file to demote this message to a WARNING. However, the use of this override is highly discouraged. These examples can be used directly in the .xdc file to override this clock rule.

< set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets CLK_IBUF] > ← Add it to the XDC file

CLK_IBUF_inst (IBUF.O) is locked to IOB_X1Y52

and CLK_IBUF_BUFG_inst (BUFG.I) is provisionally placed by clockplacer on BUFGCTRL_X0Y18


- The reason is that We bind the signal clk to a switch, which is **not** a real clock.
- see how to use a real clock in Lec04 and Lab04.

```
architecture arch_dff of D_FF is
begin
  process (clk, reset)
  begin
    if reset = '1' then
      Q <= '0';
    elsif rising_edge(clk) then
      Q <= D;
    end if;
  end process;
end arch_dff;
```


Verification on Zedboard



 - Generate the Bitstream.
- Program the Zedboard.
- Verify the functions of the SIPO shift register.
 - Test shifting by switching SW7(clk) with BTNC(reset)=0.





- Test async reset by turning on BTNC.



Little Problem: Glitch



  - If you switch once SW7 but the SIPO shifts twice, you encounter a glitch, it's OK to happen




- The glitch is caused by the poor switch contact.
 - Operating once (by human) causes multiple positive edge in the signal.
 - It is also called by switch bouncing.
- Debouncing is out of the lab03 scope.

Lab03 Requirements

Lab03: PIPO Shift Register



- Implement a **parallel-in-parallel-out (PIPO) shift register**, which is composed of **multiplexers (mux)** and **D-Flip-Flops (D-FF)** as follows:
 - It allows **parallel input** (through either external inputs (**Din**) or the shifted outputs from previous D-FFs (**Q**) based on the select signal (**sel**) at rising edges of clock (**clk**));
 - It produces **parallel output** (through external outputs (**Q**)).

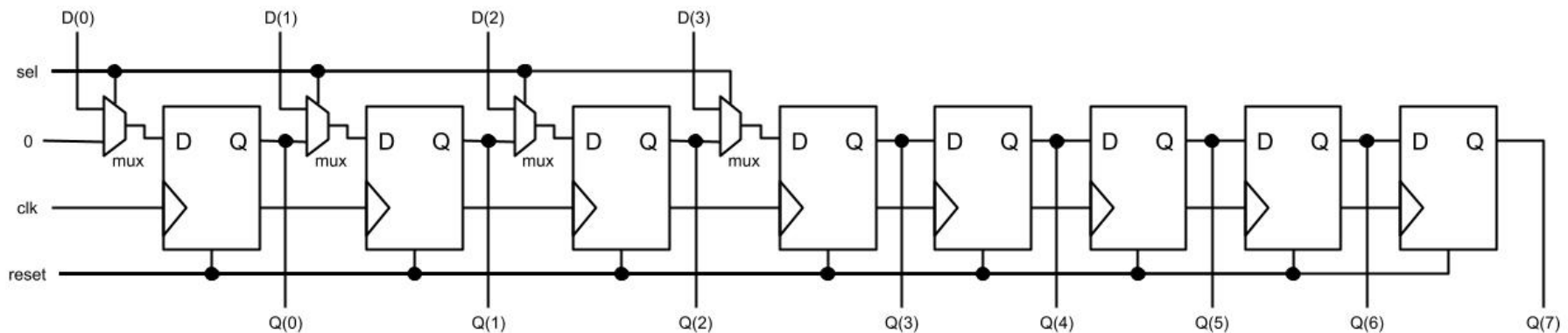

Lab03: PIPO Shift Register




- When **reset** equals to 1:
 - All the **Q(s)** are reset to zero(s) **asynchronously** (immediately).
- Otherwise (when **reset** equals to 0), at every **rising edge** of **clk**:
 - When **sel** is 1, the values of **Din** are assigned to **Q** of D-FFs in parallel;
 - Otherwise (when **sel** is 0), the value kept by each D-FF is shifted to the D-FF on its right.
 - A '0' is shifted into to the “leftmost” D-FF;
 - The value kept by the “rightmost” D-FF is shifted out (i.e., discarded) from the PIPO shift register.

Lab03: PIPO Shift Register



- Instructions:
 - Select the digit using SW 0-3
 - Press BTNU and toggle the SW7 at the same time
 - The digit will display on the LED 0-3
 - Then toggle the SW7 only
 - The digit will shift left
 - Press BTNC to reset the LED 0-7

 

Lab03: Step-by-Step Instructions (1/2)



1. Use the structural design (port map) to implement the PIPO shift register.
 - That is, implement the D-FF first, and then use D-FF to implement the PIPO shift register using port map.
 - There is no special requirement on the implementation method of multiplexers.
2. Create a XDC file with the following assignments:
 - Input: **clk** = SW7, reset = BTNC, **sel** = BTNU, **D0~D3** = SW0~SW3
 - Output: **Q0~Q7** = LD0~LD7
 - Add the following statement to your XDC file:
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_IBUF];

Lab03: Step-by-Step Instructions (2/2)



4. Generate the bitstream and download it to Zedboard.
5. Toggle SW7 regularly to simulate the **clk** and verify the behavior of your design as follows:
 - ① Set D to “0101”, press BTNU and toggle SW7;
 - ② Toggle SW7 only until “0101” move to SW4-7
 - ③ Set D to “1100”, press BTNU and toggle SW7
 - ④ Toggle SW7 several times to shift the digit
 - ⑤ Asynchronously **reset** PIPO by pressing BTNC.
 - ⑥ Record the above verification as a video for submission.
6. Submit your source code.
 - Submit the zip file of **source codes** and **verification video** to Blackboard.
 - Deadline: **14:30 on 12 Feb. 2025**
 - Late submission is NOT acceptable (unless otherwise approved)



香港中文大學
The Chinese University of Hong Kong

Thank You!

